

Hardware assignment

Name -: Shivanand Rachewad
Roll no -: BT22BTECH11014

Abstract—In this assignment we have made a Random number generator using shift registers

PROCEDURE

- 1) Connect 555 timer
- 2) Connect clock signal of D-Flip flops to the Clock output of 555 timer circuit.
- 3) The next step in the process would be to make the circuitry in such a way that shift registers for using a 4 D-Flip flops (using two 7474 IC's)
- 4) The next connection is XOR gate (7486 IC)

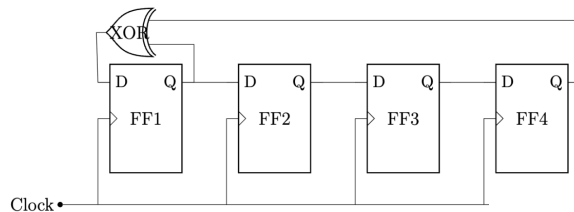


Figure 1.1.3.1: Circuit Connections

Fig. 4. circuit connection

- 5) A,B,C,D of the decoder (7447 IC) is connected with Q_0, Q_1, Q_2, Q_3 respectively

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Fig. 5. Connection of seven segmented display with decoder

- 6) Final step is to connect the seven segmented display and then connected it with the decoder (7447 IC) according to the table ?? and the figure ??
- 7) All the independent parts should be connected with each other and then connected the power source

OUTPUT

Output as expected is randomly changing numbers as per the figure ??

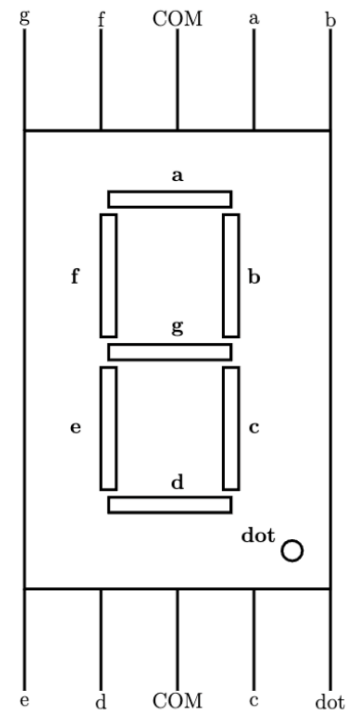


Fig. 5. Seven segmented display

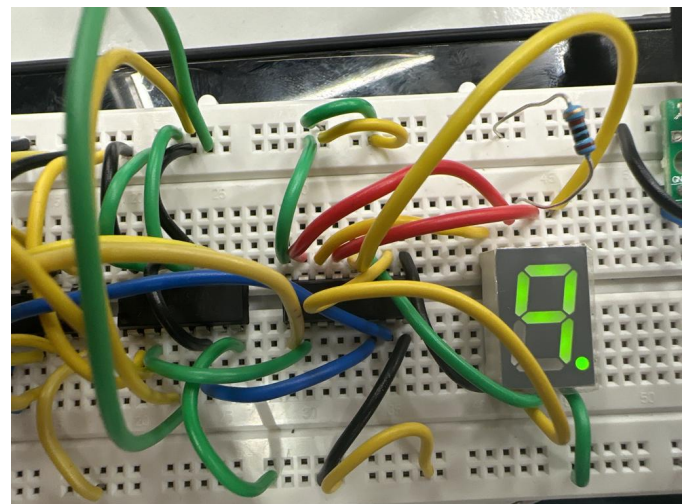


Fig. 7. output1

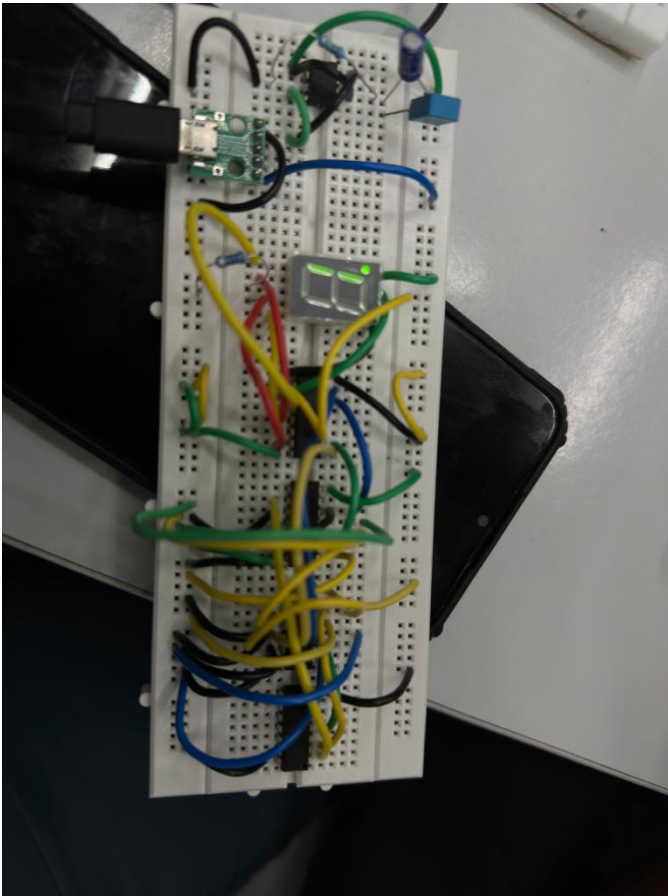


Fig. 7. output2